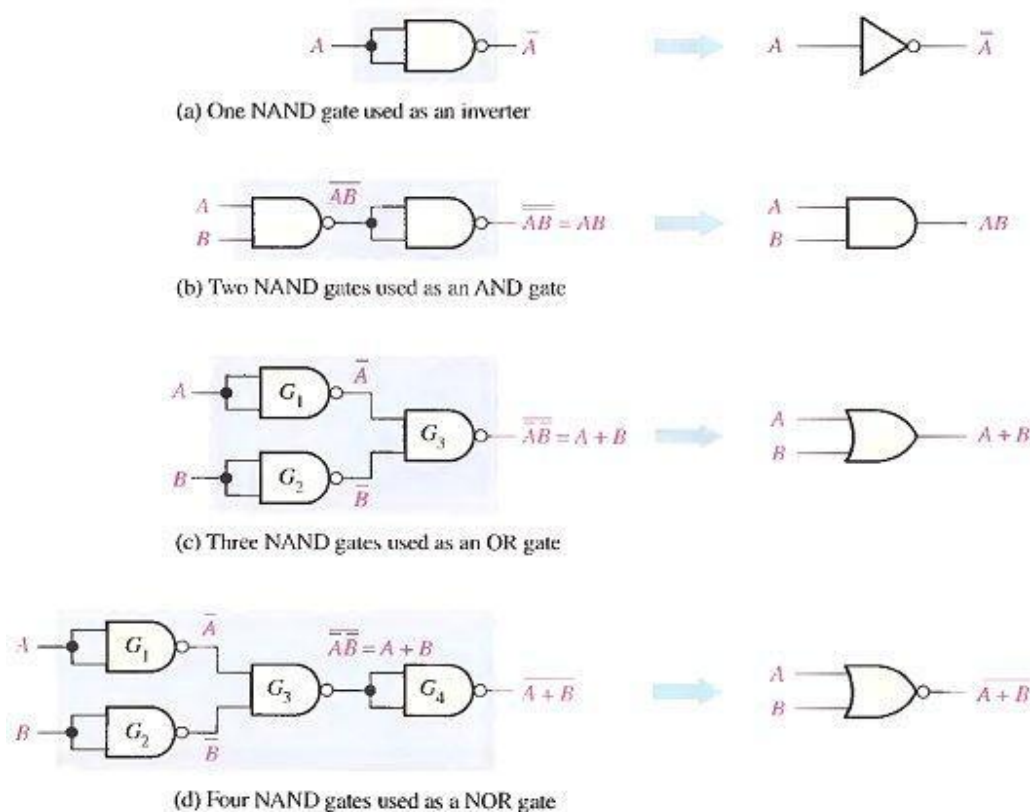


## **THE UNIVERSAL PROPERTY OF NAND AND NOR GATES**

### **1- The NAND Gate as a Universal Logic Element**

The NAND gate is a universal gate because it can be used to produce the NOT, the AND, the OR, and the NOR functions. An inverter can be made from a NAND gate by connecting all of the inputs together and creating, in effect, a single input, as shown in Fig.(6-8)(a) for a 2-input gate. An AND function can be generated by the use of NAND gates alone, as shown in Fig.(6-8)(b). An OR function can be produced with only NAND gates, as illustrated in part (c). Finally, a NOR function is produced as shown in part (d).




**Fig.(6-9)**

## 2- The NOR Gate as a Universal Logic Element

Like the NAND gate, the NOR gate can be used to produce the NOT, AND, OR and NAND functions. A NOT circuit, or inverter, can be made from a NOR gate by connecting all of the inputs together to effectively create a single input, as shown in Fig.(6-10)(a) with a 2-input example. Also, an OR gate can be produced from NOR gates, as illustrated in Fig.(6-10)(b). An AND gate can be constructed by the use of NOR gates, as shown in Fig.(6-10)(c). In this case the NOR gates G 1 and G 2 are used as inverters, and the final output is derived by the use of DeMorgan's theorem as follows:

$$X = A + B = \overline{\overline{A + B}} = \overline{\overline{A} \cdot \overline{B}}$$

Fig.(6-10)(d) shows how NOR gates are used to form a NAND function.

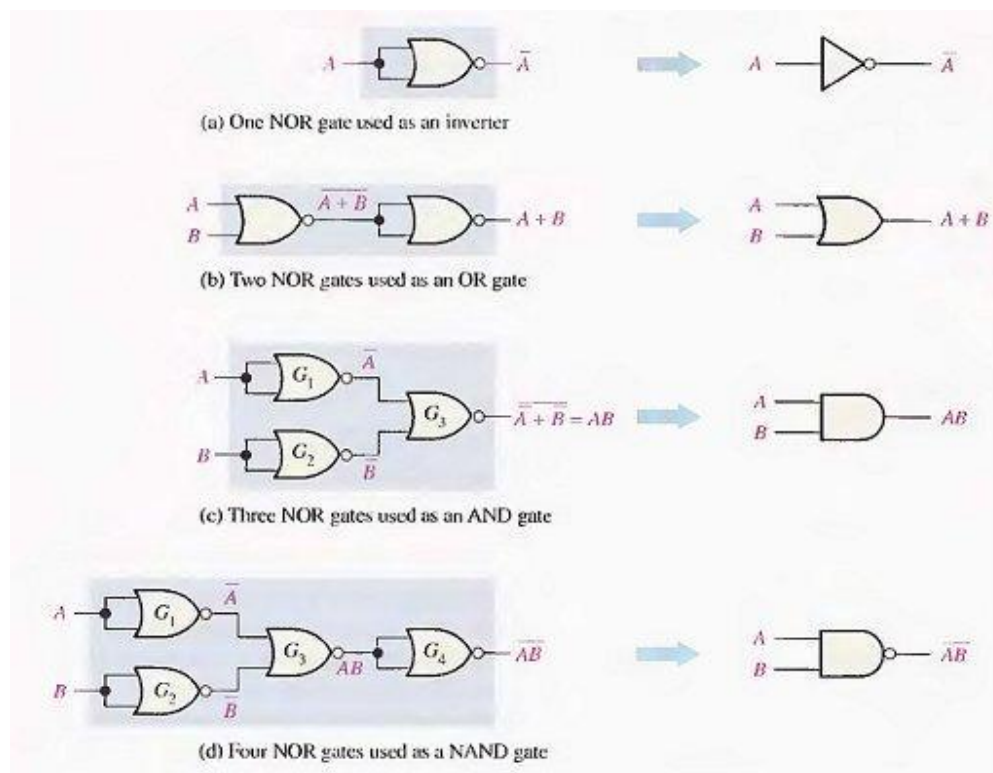

**Fig.(6-10)**

### Example

1. Use NAND gates to implement each expression:  
(a)  $X = \bar{A} + B$       (b)  $X = A\bar{B}$
2. Use NOR gates to implement each expression:  
(a)  $X = \bar{A} + B$       (b)  $X = A\bar{B}$

### Example

- 1- Write the output expression for each circuit as it appears in Fig.(6-11) and then change each circuit to an equivalent AND-OR configuration.
- 2- Develop the truth table for circuit in Fig.(6-11)(a-b).
- 3- Show that an exclusive-NOR circuit produces a POS output.

